

**Aim of the Experiment:** To design a quarter wave transformer for matching a 50 Ohm microstrip line with a load of **115 Ohms**.

**Software to be used:** CST studio suite 2019 (Student edition)

**Design:**

- **Mathematical Calculation**

When  $l = \lambda/4$ , we have the below equation (equation 1)

$$Z_{in} = Z_o \left[ \frac{Z_L + jZ_o \tan(\pi/2)}{Z_o + jZ_L \tan(\pi/2)} \right] = \frac{Z_o^2}{Z_L}$$


From equation (1),  $Z_o^l$  is selected such that ( $Z_{in} = Z_o$ ), (equation 2),

$$\therefore Z_o^l = \sqrt{Z_o \cdot Z_L} = \sqrt{50 \times (115)} = 75.828 \text{ Ohms}$$


When microstrip line is used, then guided wavelength must be, (equation 3)

$$\lambda_g = \frac{\lambda_o}{\sqrt{\epsilon_{eff}}}$$

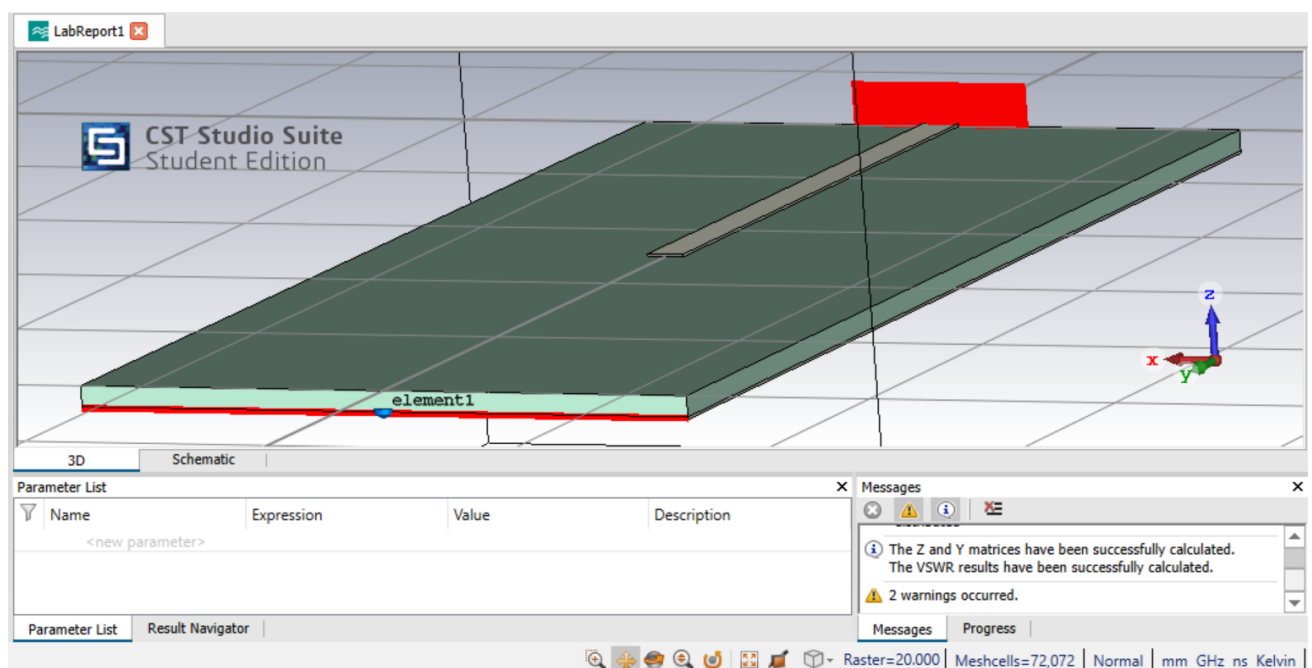
- **Design of microstrip line terminated with the desired load**



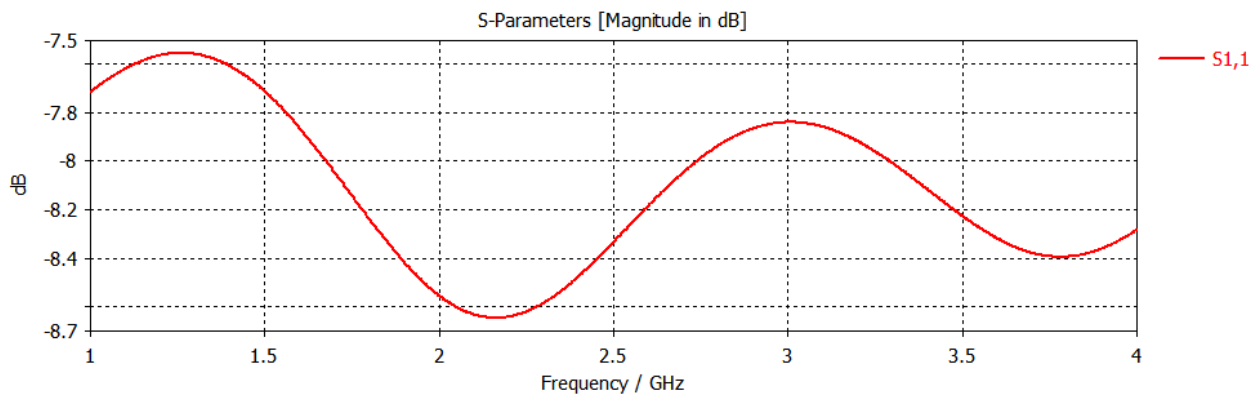
- S11 characteristics of the microstrip line terminated with the load



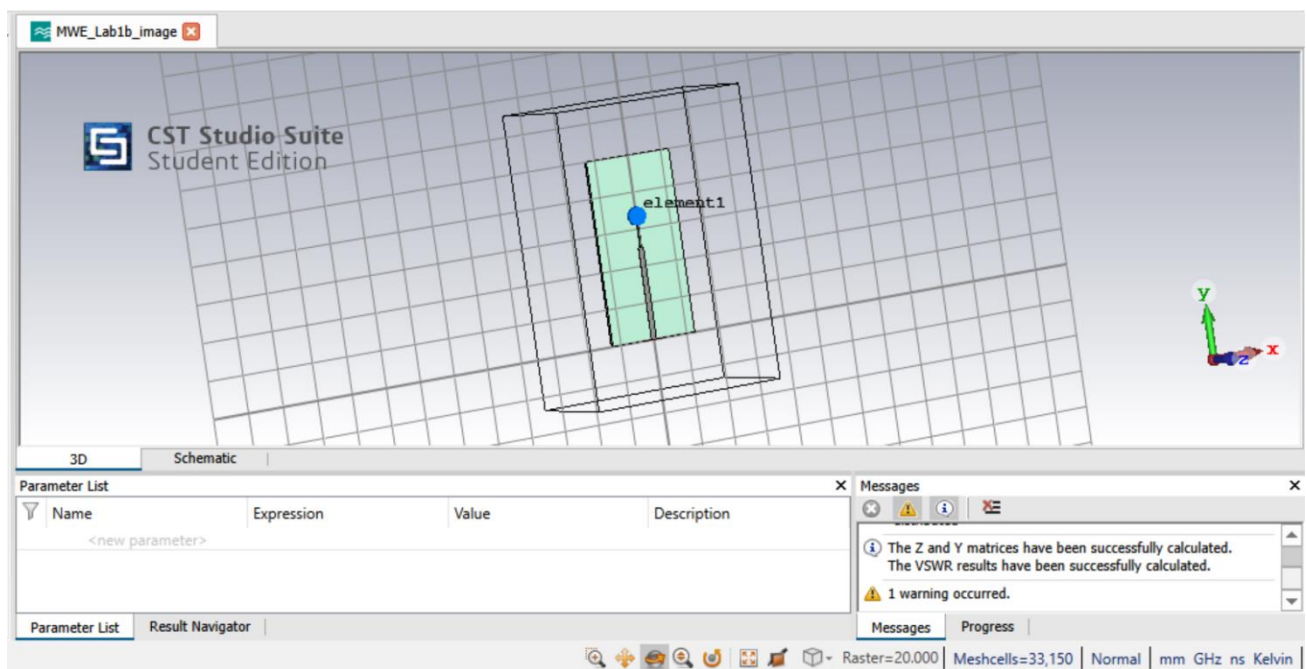- Design of microstrip line terminated with quarter wave line and the desired load



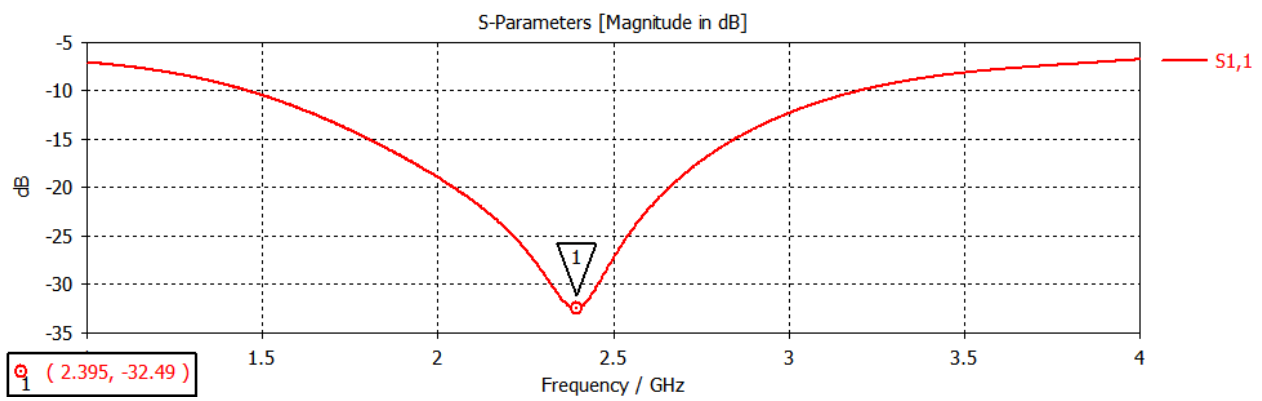- S11 characteristics of the microstrip line terminated with quarter wave line and the desired load



### ***Conclusion***

The quarter wave transformer with a load of 115 Ohms was designed for matching a 50 Ohms microstrip line. An impedance match is achieved at 2.39 GHz by using the aforementioned quarter wave transformer.

Name: Rishabh Panda

Roll Number: 1904215

Section: ETC 3